

Diode Problems (10) — Problems Only

1. 1) (Ideal diode) For the circuit shown: a sinusoidal source $v_s(t)=10\sin(\omega t)$ V in series with a diode and a $1\text{k}\Omega$ resistor to ground. Sketch $v_o(t)$ across the resistor using the ideal diode model. What is the peak output voltage?
2. 2) (Half-wave rectifier with load) A diode in series with a 100Ω load is driven by $v_s(t)=20\sin(1000t)$ V. Assuming an ideal diode, find the DC (average) output voltage across the load.
3. 3) (Diode with DC bias) A diode (ideal) is connected between a 5 V DC source and a resistor $R=2\text{k}\Omega$ to ground as: +5V \rightarrow diode (anode at +5V) \rightarrow node V_o \rightarrow R to ground. Find V_o .
4. 4) (Clipper - positive) Design a diode clipper that limits the output to $\pm 3\text{V}$ using ideal diodes and a $\pm 12\text{V}$ input. Sketch the transfer behavior and explain operation.
5. 5) (Clamper) A series capacitor $C=1\mu\text{F}$, diode (ideal), and $10\text{k}\Omega$ load form a positive clamper. Input is $v_s(t)=5\sin(2\pi 1000t)$ V. Describe qualitatively how the DC level of the output shifts and why.
6. 6) (Diode with threshold) Replace the diode by a silicon diode with $V_\gamma=0.7\text{V}$ in problem (1). For $v_s(t)=10\sin(\omega t)$, what is the peak output approximately?
7. 7) (Bridge rectifier + capacitor filter) A full-wave bridge fed from 12VAC RMS transformer (ideal), load $R=1\text{k}\Omega$, filter C large. Estimate the DC output (approx) after the filter and peak-to-peak ripple (approx).
8. 8) (Piecewise linear analysis) For circuit: 10V source \rightarrow series $1\text{k}\Omega$ resistor \rightarrow diode (ideal) \rightarrow $2\text{k}\Omega$ to ground. Find V_o at node between diode and $2\text{k}\Omega$. Determine conduction state and numeric V_o .
9. 9) (Two-diode limiter) Two identical diodes in opposite directions (ideal) in series with $1\text{k}\Omega$ to ground form a limiter driven by $\pm 15\text{V}$ source. Sketch V_{out} and find thresholds.
10. 10) (Temperature/real diode) Brief conceptual: how does junction temperature affect the forward voltage and leakage current of a silicon diode? Explain consequences for precision circuits.